

Roll No.

Total No. of Questions : 09]

[Total No. of Pages : 02

B. Tech. ECE/ETE (Sem. - 3rd)

ANALOG DEVICES AND CIRCUITS

SUBJECT CODE : BTEC-301 (2011 & 2012 Batch)

Paper ID : [A1130]

Time : 03 Hours

Maximum Marks : 60

Instruction to Candidates:

- 1) Section - A is compulsory consisting of Ten questions carrying Two marks each.
- 2) Section - B contains Five questions carrying Five marks each and students has to attempt any Four questions.
- 3) Section - C contains Three questions carrying Ten marks each and students has to attempt any Two questions.

Section - A

Q1)

- a) Differentiate between LEDs and Photodiode.
- b) A Silicon diode is connected in series with a load resistance of 10 ohm. For a dc supply of 5 V, determine the current in the circuit.
- c) Explain how transistor acts as an amplifier?
- d) What is UJT? Give its various applications.
- e) What is cross over distortion
- f) List various drawbacks of complementary symmetry amplifier.
- g) Explain feedback factor and open loop gain
- h) What are the limitations of h parameters?
- i) Compare Wein Bridge Oscillators and RC Phase Shift Oscillators.
- j) Draw the hybrid model of CE BJT and define h_{fe} and h_{oe} .

R-1910

P.T.O.

Section - B

- Q2) Derive the relation between maximum power and transistor dissipation for class B push pull amplifier.
- Q3) Discuss the effect of temperature on PN junction diode.
- Q4) A transistor is operated in CE configuration. If α is 0.99, I_{CBO} is 10 micro amperes and I_B is 200 micro amperes. Calculate β , I_C and I_E . Also draw the circuit diagram.
- Q5) Discuss with the help of circuit diagrams the purpose of providing negative and positive feedback.
- Q6) Explain briefly the working of Hartley oscillator and also derive the expression for frequency of oscillations.

Section - C

- Q7) Give the need of biasing. Discuss different methods by which it is achieved for a NPN BJT?
- Q8) Explain working and characteristics of JFET. How does it differ from BJT?
- Q9) Write short notes on any two of the following:
- i) High frequency T model
 - ii) Zener diode as voltage regulator
 - iii) Effect of negative feedback on bandwidth

