

Roll No.

Total No. of Questions : 09]

[Total No. of Pages : 02

B.Tech. (ECE/Electronics & Computer Engg./ ETE) (Sem. - 3rd)

NETWORK ANALYSIS AND SYNTHESIS

SUBJECT CODE : BTEC - 303 (2011 & 2012 Batch)

Paper ID : [A1127]

Time : 03 Hours

Maximum Marks : 60


Instruction to Candidates:

- 1) Section - A is **Compulsory** consisting of ten questions carrying two marks each.
- 2) Section - B contains **Five** questions carrying **Five** marks each and students has to attempt any four questions.
- 3) Section - C contains **Three** questions carrying **Ten** marks each and students has to attempt any two questions.

Section - A

Q1)

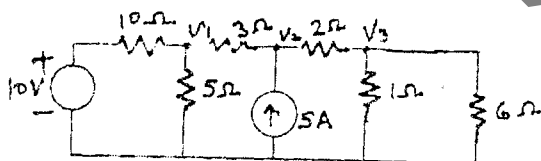- a) What is meant by the term transients? Draw the transient response of R-L series circuits.
- b) State Reciprocity theorem. Give example.
- c) Classify different types of network elements.
- d) Write the nodal equations for the following circuit.




- e) Explain convolution theorem.
- f) What are composite filters. How they are better than prototype and m-derived filters.
- g) What are transfer functions? Give its significance.
- h) Explain the behavior of an inductor at $t = 0$ and $t = \infty$ when there is initial current in it.
- i) What is meant by analysis and synthesis of a network.
- j) Differentiate between prototype filter and m-derived filters.

Section - B

Q2) Explain time domain response from pole and zero plot. Plot the poles and zeros of a network function on the s-plane.

$N(s) = (s + 1)(s + 5)(s + 3 + 2j)(s + 3 - 2j)$ and check the stability of the system.

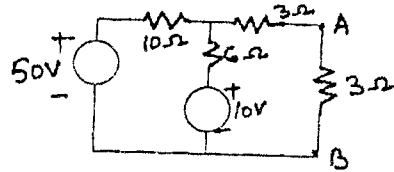Q3) State Thevenin theorem. Find the current flowing in branch AB using thevenin theorem.



Q4) Find the voltage across capacitor C_1 .



Q5) Test whether the polynomial $P(s) = S^3 + 4S^2 + 5S + 2$ is Hurwitz.

Q6) Derive the Laplace transform of step, ramp, impulse and unit doublet function.


Section - C

Q7) Find the first and second Foster forms of the function

$$Z(s) = (s + 1)(s + 3) / s(s + 2)$$

Q8) Explain different characteristics of filters. Derive equations of Characteristics impedance, Propagation constant, attenuation and phase shift of T-network.

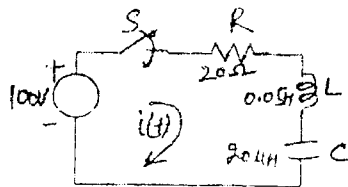Q9) Determine the current $i(t)$ in the given circuit when the switch is closed at $t = 0$.



XXXXX