

Roll No. ....

Total No. of Questions : 09]

[Total No. of Pages : 02

**B.Tech. (ETE/ECE/Electronics & Computer Engg.) (Sem. - 5<sup>th</sup>)**

**LINEAR INTEGRATED CIRCUITS**

**SUBJECT CODE : BTEC - 503 (2011 Batch)**

**Paper ID : [A2105]**

**Time : 03 Hours**

**Maximum Marks : 60**

**Instruction to Candidates:**

- 1) Section - A is compulsory consisting of Ten questions carrying Two marks each.
- 2) Section - B contains Five questions carrying Five marks each and students has to attempt any Four questions.
- 3) Section - C contains Three questions carrying Ten marks each and students has to attempt any Two questions.

**Section - A**

- Q1)** a) What is the expression for voltage gain of DIBO differential amplifier with swamping resistors?
- b) List the ideal characteristics of an Op-Amp.
- c) What are the limitations of the basic differentiator circuit?
- d) What is a Schmitt trigger?
- e) Draw a well labeled transfer curve of an Op-amp?
- f) Define CMMR and PSRR.
- g) A three-pole high-pass active filter would have a roll-off rate of:
- i) 40 dB/decade
  - ii) -40 dB/decade
  - iii) -60 dB/decade
  - iv) -20 dB/decade
- h) Define input offset voltage. State the reasons for the offset voltages of the op-amp.
- i) Draw the labelled pin diagram of 555 timer IC.
- j) Distinguish between active and passive filters.

### Section - B

- Q2) Discuss the current mirror circuit. How is it helpful in improving the CMRR?
- Q3) Describe the application of OP-AMP as current voltage converter.
- Q4) What is slew rate? What are its causes? Derive the expression of maximum frequency of operation for a desired output swing in terms of slew rate.
- Q5) Derive the expression for voltage as a function of frequency. Define break frequency and bandwidth.
- Q6) Describe the operating principle of PLL. Define capture range and locking range.

### Section - C

- Q7) Describe the working of practical differentiator circuit. Derive the expression for output voltage. Also discuss the frequency response of the differentiator.
- Q8) Describe the applications of OP-AMP in open loop configuration.
- Q9) Write short notes on the following :
- a) VCO
  - b) Triangular wave generator.

