

Roll No.....

Total No of Pages-02

Examination May –2014
BTEC-303: NETWORK ANALYSIS AND SYNTHESIS
Paper ID : A1127

Time Allowed: 3 Hours.

Max Marks – 60

Instructions to Candidates:

1. Section-A is compulsory consisting of ten questions carrying Two marks each.
2. Section-B contains Five questions carrying Five marks each and student has to attempt any Four questions.
3. Section-C contains Three questions carrying Ten marks each and student has to attempt any two questions.

Section –A

(10X2= 20 Marks)

- Q.1
- a) State Thevenin's theorem.
 - b) Find the energy stored in the inductor of a coil having $R=10\Omega$ and $L=15H$ at the instant when the current is 10A and increasing @5A/sec.
 - c) Obtain the Laplace transform of $f(t)=1-e^{at}$, a being a constant.
 - d) Show the derivative of an unit ramp function is a step function.
 - e) State the condition for any active network or a general system to be a strictly stable system.
 - f) Check whether the polynomial $S^8+S^7+S^6-2S^5+4S^3+S^2+S+1$ is Hurwitz or not.
 - g) Which property of reactive network is referred to as the separation property.
 - h) Explain the homogeneity property of superposition theorem.
 - i) Give relationship between neper and decibel.
 - j) What are terminating half sections?

Section –B

(4X5=20 Marks)


- Q.2 The driving point impedance of a one port LC network is given by
- $$Z(s)=5\{s(s^2+4)\}/\{(s^2+1)(s^2+9)\}$$
- Obtain the first and second Foster form of equivalent network.
- Q.3 What are composite filters? Why are they needed? Give block diagram representation of composite filter. Also derive the value of m at which terminating half sections should be designed.

- Q.4 Give the restriction on the locations of poles and zeros in the transfer functions.
- Q.5 State and Prove Superposition Theorem.
- Q.6 Apply Routh Criterion to the following equation and determine the number of roots (i) with positive real parts (ii) with zero parts (iii) with negative real parts.
 $S^5 + S^4 + 4S^3 + 24S^2 + 3S + 63 = 0$

Section -C

(2X10=20 Marks)

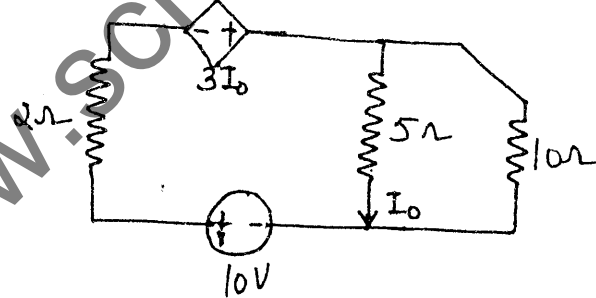- Q.7 What is a filter? Give the properties of filter? Classify the filters depending upon the relationship between the arm impedance. Derive the expressions for β , α and characteristic impedance of a filter in the pass band and stop band.
- Q.8 Discuss the conditions under which a passive two port network is reciprocal and symmetrical. Let the transform current $I(S)$ in a network be given by $I(S) = 2s / \{(s+1)(s+2)\}$ plot the poles and zeros in the s-plane and hence obtain the time domain response.
- Q.9 Find the current through 10Ω resistor in the given circuit using (i) Thevenin's theorem (ii) Norton's theorem.



-----End-----