

Roll No _____

Total No of pg: 1

Examination May-2014
PULSE WAVE SHAPING AND SWITCHING
B. Tech
Subject Code: BTEC405
Paper ID: A1193

Time : 03 Hrs.

Max. Marks: 60

SECTION – A

Compulsory

(2x10=20)

1.
 - a) What is delay time of a transistor? What factors does contribute to it?
 - b) What do you mean by biased clamping?
 - c) Define operational amplifier Comparator?
 - d) How a High R C circuit is used in Linear Waveshaping?
 - e) What are Passive and Active Circuit elements?
 - f) Why is the Capacitor in an R C high pass circuit called a blocking Capacitor?
 - g) Define upper tripping point and cover tripping point?
 - h) What is Camparator? How it is used?
 - i) Define the turmo ac Coupling and dc Coupling in Multiviberator?
 - j) What is slicer?

SECTION – B

Attempt any Four questions

(4x5=20)

2. Explain Fixed bias and self-bias bistable Multivibrator?
3. Derive Resonant frequency and Impedence of a parallel tuned Circuits with its Phasor Diagram?
4. What is blocked Condition in an alstable multivibrator? How to overcome it? Show how as table multivibrator can be used as a Voltage to frequency converter?
5. Explain Charge storage phenomena?
6. Why a charge Compensating Capacitor is used in diode switch?

SECTION – C

Attempt any Two questions

(10x2=20)

7.
 - a) With the help of neat circuit diagram and waveforms, explain the working of Schmitt trigger.
 - b) How can hystensis be eliminated in Schmitt trigger?
8.
 - a) Derive the expression for gate width of a Monostable Multiviberator considering the effect of Revenues saturation current?
 - b) Explain breakdown mechanism in diode?
9.
 - a) Draw the Circuit Diagram of double diode clipper which limits at two independent levels and explain it with its transfer characteristic.
 - b) What are different schemes for temperature compensation of a clipper? Explain them briefly?

.....End.....