

**Examination May-2014**

**B.Tech-ECE**  
**VLSI DESIGN**  
**Subject Code: BTEC-604**

**Time: 03 Hours****Maximum Marks: 60****Instruction to Candidates:**

**Section-A** is compulsory consisting of ten questions carrying two marks each.

**Section-B** consists of five questions carrying five marks each and students have to attempt any four questions.

**Section-C** contains three questions carrying ten marks each and students have to attempt any two questions.

**Section-A**

1.

- a) What are various capabilities of VHDL?
- b) Explain VHDL design flow with an example?
- c) Explain various multiplying operators in VHDL with examples?
- d) How does PLA different from ROM?
- e) Define Generate, Guarded Block, and Assert statements in VHDL.
- f) Differentiate between behavioral and dataflow style of circuit modeling.
- g) What are various CAD tools for digital circuit design?
- h) What are PULL UP and PULL DOWN networks?
- i) What are transport and inertial delays in VHDL?
- j) What are Generics?

**Section-B**

2. Design a Full adder using two half adders. Implement this Full adder using VHDL Code.
3. Write a VHDL Code to implement the function
$$f(x_1, \dots, x_4) = \prod M(3, 11, 14) + \sum D(0, 2, 10, 12).$$
4. Write a VHDL code for BCD to 7- Segment decoder using CASE statement.

5. Write a VHDL description of the following combinational network in Fig.1 concurrent statements. Each gate has a 5-ns delay, excluding the inverter, which 2-ns delay.

 


Fig.1

6. Write VHDL Code using behavioral modeling style that represents a T-flip- flo an asynchronous clear input.

### Section-C

7. a) Implement the CPU of a basic computer using VHDL. This CPU is to perform least arithmetic and logical functions on an 8-bit data.  
b) What are programmable logic devices? Explain architecture of a general FPGA
8. Design a 3- bit UP/Down counter using T-Flip Flops. It should include a control called  $\overline{UP}/Down$ . If  $\overline{UP}/Down = 0$ , then the circuit should behave as an up-counter. If  $\overline{UP}/Down = 1$ , then the circuit should behave as a down counter. Implement this UP/Down Counter using VHDL Code.
9. Draw the CMOS inverter and discuss its DC characteristics. Write the conditions for different regions of operation.

————— End —————