

**Total No. of Questions : 09**

Total No. of Pages : 02

# NETWORK ANALYSIS AND SYNTHESIS

**Subject Code : BTEC-303**

Paper ID : [A1127]

**Time : 3 Hrs.**

**Max. Marks : 60**

**INSTRUCTION TO CANDIDATES :**

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains FIVE questions carrying FIVE marks each and students has to attempt any FOUR questions.
3. SECTION-C contains THREE questions carrying TEN marks each and students has to attempt any TWO questions.

## SECTION-A

1. Write briefly :
- (a) Explain the term Network Synthesis.
  - (b) What are Dependent Sources ? Explain with example.
  - (c) Define Superposition theorem.
  - (d) State and explain Maximum Power Theorem.
  - (e) Define Ideal Filter.
  - (f) Differentiate between loop and mesh.
  - (g) What is the need of Laplace transform ?
  - (h) List the demerits of m-derived filters.
  - (i) Define positive real function.
  - (j) How will you define transfer function? Explain.

## SECTION-B

2. State and prove convolution theorem.
3. An impedance function is given by

$$Z(s) = \frac{2(s+1)(s+3)}{(s+2)(s+4)}$$

Find the RL representation of foster first form of network.

4. (a) How can you remove a pole at infinity ?  
(b) How can you remove a pole at zero ?  
(c) What are the necessary conditions of stability of a network function ?
5. Discuss realizability conditions for impedance synthesis of RL and RC circuits.
6. How is open circuit (Z) parameters converted into short circuit (Y) - parameters? Show all steps involved and discuss conditions for reciprocity and symmetry.

#### SECTION-C

7. Define driving point impedance and admittance. State restrictions on location of poles and zeros in driving point functions. What are the various necessary conditions for transfer condition ?
8. Design a low pass prototype T-section filter having cut off frequency of 2 KHz to operate with a terminated load resistance of 500 ohm.
9. Draw m-derived high pass filter. Plot characteristic impedance, phase shift and attenuation *verses* frequency for m-derived filter.