

Total No. of Questions : 09

Total No. of Pages : 02

B.Tech.(ECE / ETE) (2011 Onwards) (Sem.-4)
PULSE WAVE SHAPING AND ANALYSIS

PULSE WAVE SHAPING AND SWITCHING (Sem.-
Subject Code: 5770

Subject Code : BTEC-405

Paper ID : [A1193]

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTIONS TO CANDIDATES :
1. SECTION A : 100

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains FIVE questions carrying FIVE marks each and students have to attempt any FOUR questions.
3. SECTION-C contains THREE questions carrying TEN marks each and students have to attempt any TWO questions.

SECTION-A

1. Write briefly :

- Write briefly effect of temperature on diode.
- Mention the names and compare active and passive circuit elements.
- What do you understand by positive feedback? Where is it useful?
- Give technique to improve the switching speed BJT transistor.
- Draw circuit diagram of 5 volt clamper?
- Draw the output wave form of High pass filter for the input of sinusoidal output.
- Define the condition for High Pass Filter to act as good differentiator.
- Distinguish monostable and bistable multivibrator.
- Sketch the ringing circuit.
- Give a shortcoming of operating a transistor in saturation region.

SECTION-B

- 2) Define various input signals

- i) Sinusoidal
- ii) Exponential
- iii) Ramp
- iv) Unit Step.

How does a nonlinear circuit behave for each of them?

- 3) Explain the working of Transistor Switch with Inductive Load.
- 4) Prove that Gate width (T) of a Collector Coupled Monostable multivibrator is $T = \tau \ln 2$. Symbols have usual meaning.
- 5) Explain the working of Operational amplifier based comparator.
- 6) Draw and explain the working of double differentiator circuit. Find its output, in case of exponentially rising input.

SECTION-C

- 7) a) Define and explain triggering and its types used in multivibrators. 5
- b) Refer to **Figure 1**, A collector coupled one shot using p-n-p germanium transistors has the following parameters : $V_{cc} = -3V$, $V_{BB} = 9V$, $R = 2.7K$, $R_c = 270\Omega$, $R_1 = 1K$, $R_2 = 15K$, $h_{FE} = 25$, $C = 0.01\mu F$. Neglect saturation junction voltages and r_{bb} . Calculate and plot to scale the waveshapes at each base and collector. 5

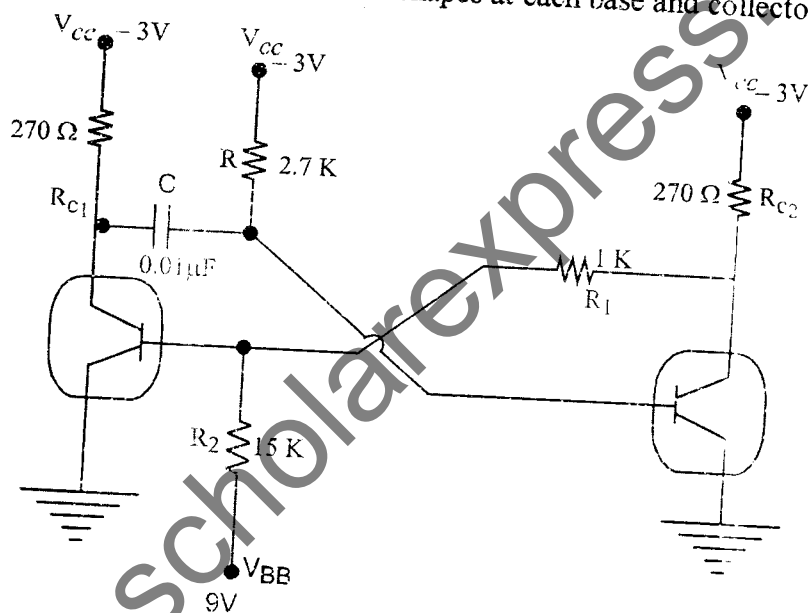


Figure 1

- 8) a) Calculate the RMS and Average value of a sinusoidal waveform over a half cycle. 5
- b) Explain the working and applications of Schmidt trigger circuit. 5
- 9) Write short note on the following :
 - a) Clamping circuit theorem 3
 - b) Applications of Voltage Comparator 3
 - c) Various times concerned with transistor switching. 4